

ELECTROTECHNICS SOLUTION HTTC BAMBILI 2009

EXERCISE 1 :


Data : $P=50\text{Hp}$;

$U=575\text{V}$; $p=2$; $f=60\text{Hz}$; $R_1=0.17\Omega$; $R_2=0.24\Omega$; $X_1=0.55\Omega$; $X_2=0.6\Omega$; $I_0=18\text{A}$;

$P_0=2490\text{W}$

1.1- For $g=0.033$, $P_{\text{fer}}=P_{\text{rot}}$ determine :

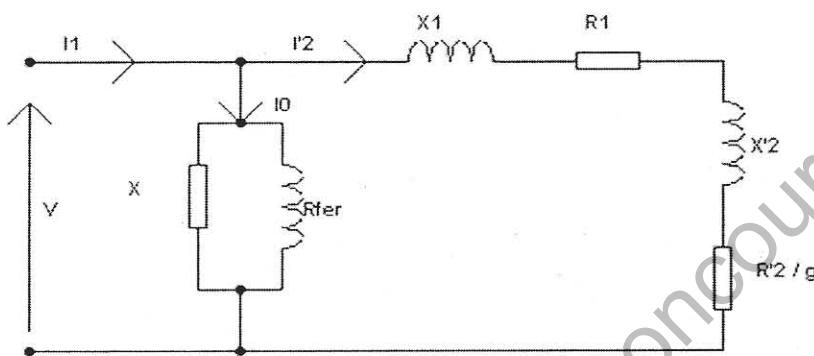1.1.1- The value of the current and power factor



• **Value of the current I_1**

$$\underline{I_1} = \underline{I_2} + \underline{I_0} ;$$

$$\underline{I_2'} = \frac{V}{\left(R_1 + \frac{R_2}{g}\right) + j(X_1 + X_2')} = \frac{575/\sqrt{3}}{\left(0.17 + \frac{0.24}{0.033}\right) + j(0.55 + 0.6)}$$

$$= \frac{331.976}{7.442 + j1.16}$$

$$\underline{I_2'} = 44.087 \angle -8.78^\circ \text{ (A)}$$

$$I_0 = 18\text{A}$$

$$\text{But } P_0 = 3VI_0 \cos \phi_0 \rightarrow \cos \phi_0 = \frac{P_0}{3V.I_0}$$

$$\cos \phi_0 = \frac{2490}{3 \times 331.976 \times 18} = 0.1388 \rightarrow \phi_0 = 82.01^\circ ;$$

Then

$$\underline{I}_1 = \underline{I}_2 + \underline{I}_0 = 44.087 \angle -8.78^\circ + 18 \angle 82.01^\circ ;$$

$$\underline{I}_1 = 43.57 - j6.729 + 2.502 + j17.82 ;$$

$$\underline{I}_1 = 46.07 + j11.091 = 47.388 \angle 13.53^\circ ;$$

$$\underline{I}_1 = 47.388 \angle 13.53^\circ (A)$$

- Power factor

$$\underline{I}_1 = 47.388 \angle 13.53^\circ (A) \rightarrow \cos \varphi = \cos(13.53) = 0.972$$

$$\cos = 0.972; \text{ Leading}$$

1.1.2- Developed torque

The developed power is

$$P_2 = 3 \cdot I_2'^2 \left(\frac{R_2'}{g} \right) ;$$

So

$$T_2 = \frac{P_2}{2\pi N_s}$$

Then


$$P_2 = 3 \cdot 44.087^2 \left(\frac{0.24}{0.03} \right) = 42407.20W$$

And then since $f=60\text{Hz}$ and $p=2 \rightarrow N_s = \frac{f}{p} = \frac{60}{2} ; N_s = 30\text{rps} = 1800\text{rev/min}$

$$T_2 = \frac{P_2}{2\pi N_s} = \frac{60 \times 42407.20}{2\pi \times 1800} ;$$

$$T_2 = 225.09Nm$$

1.1.3- Mechanical power P_m

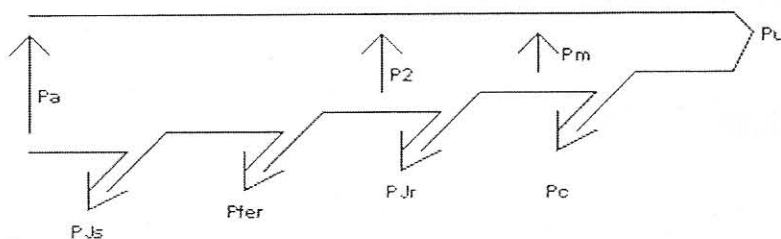

$$P_m = P_2 - P_{jr} = P_2 - g.P_2 = (1-g)P_2 ;$$

$$P_m = (1-g)P_2$$

$$P_m = (1-0.033)42407.20 ;$$

$$P_m = 41007.7624W$$

1.1.4- The efficiency

$$\eta = \frac{P_u}{P_a} = \frac{P_u}{P_2 + P_{fer} + P_{js}} ;$$

$$\text{but } P_{fer} = P_{rot} = gP_2 = 0.033 \times 42407.20 = 1399.43$$

$$\text{and } P_{js} = 3R_1 I_1^2 = 3 \times 0.17 \times 47.388^2 = 1145.26W$$

$$\eta = \frac{50 \times 736}{42407.20 + 1145.26 + 1399.43} ;$$

$$\eta = 81.86\%$$

1.2- Calculation of the current at starting (I_{st})

At starting $N=0 \rightarrow g = 1$

$$I_{2st} = \frac{V}{\sqrt{(R_1 + R'_2)^2 + (X_1 + X'_2)^2}} = 271.91 \angle 70.38^\circ$$

$$I_0 = 18 \angle 82.01^\circ$$

$$\text{Then } \vec{I}_{st} = \vec{I}_{2st} + \vec{I}_0 ;$$

$$\vec{I}_{st} = 289.56 \angle 71.1^\circ (A)$$

EXERCISE 2

Data:

- 10 pump: 0.75KW, $\cos\phi=0.75$, $\eta=0.76$

$$8 \text{ pump: } 3KW, \cos\phi=0.8, \eta=0.87$$

$$K_u=0.9 ; K_s=0.9$$

- 15 three phase resistor: 2KW

$$K_u=1 ; K_s=1$$

I- Determine the circuit breaker current Q_1 , Q_2 , and Q_3

• Power on Q_2 line

Appliance	P_u (KW)	η	K_u	K_s	$\cos\phi$	$P_a(KW)$	$Q_a(KVAR)$
10pumps Of 1.75KW Each	7.5	0.76	0.9	0.9	0.75	08	7.05
08 pumps Of 3KW each	24	0.87	0.9	0.9	0.8	22.35	16.76
					Total	30.55	23.81

$$S_{Q_2} = \sqrt{P_a^2 + Q_a^2} = \sqrt{30.35^2 + 23.81^2} = 38.575$$

$$S_{Q_2} = 38.575 \text{ KVA} \rightarrow I_{Q_2} = \frac{S_{Q_2}}{\sqrt{3}U} = 101.2; \quad I_{Q_2} = 101.23 \text{ A}$$

• Power on Q_3 line

Appliance	P_u (KW)	η	K_u	K_s	$\cos\phi$	$P_a(KW)$	$Q(KVAR)$
15 3~ Resistance 2KW	30	1	1	1	1	30	00

$$S_{Q_3} = 30 \text{ KVA}$$

$$I_{Q_3} = \frac{S_{Q_3}}{\sqrt{3}U} ; = \frac{30000}{\sqrt{3} \times 220} = 78.73 \text{ A} ; \quad I_{Q_3} = 78.73 \text{ A}$$

• Power on Q_1 line

$$S_{Q_1} = \sqrt{(P_{ap} + P_{aR})^2 + Q_p^2} ; = \sqrt{(30.35 + 30)^2 + (23.81)^2} = 64.877 \text{ KVA}$$

$$I_{Q_1} = \frac{S_{Q_1}}{\sqrt{3}U}$$

$$= \frac{64877}{\sqrt{3} \times 220} = 170.25A ;$$

$$I_{Q_1} = 170.25A$$

EXERCISE 3:

3.1 Determination of the total apparent power (S_T)

Receptor (A)

$$P_A = S_A \cos \varphi$$

$$P_A = 15 \times 0.6 ;$$

$$P_A = 9KW$$

$$Q_A = S_A \sin(\cos^{-1} 0.6)$$

$$Q_A = 15 \times 0.8 ;$$

$$Q_A = 12KVAR$$

Receptor (B)

$$P_B = S_B \cos \varphi$$

$$P_A = 12 \times 0.9 ;$$

$$P_A = 10.8KW$$

$$Q_B = S_B \sin(\cos^{-1} \varphi)$$

$$Q_A = 12 \times \sin(\cos^{-1} 0.9) ;$$

$$Q_A = 5.23KVAR$$

Load	KW	KVAR
A	9	12
B	10.8	5.23
Total	19.8	17.23

Therefore

$$S_T = \sqrt{P_{AB}^2 + Q_{AB}^2} ; S_T = \sqrt{19.8^2 + 17.23^2} = 26.25KW ;$$

$$S_T = 26.25KW$$

3.2 Determination of the power factor


$$\cos\varphi = \frac{P_{AB}}{S_T}$$

$$;\cos\varphi = \frac{19.8}{26.25};$$

$$\cos\varphi = 0.75$$

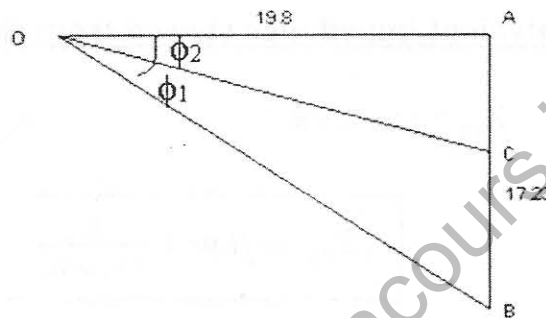3.3 To raise the power factor to 0.98

- Determination of the set reactive power



As previously determined,

$$AB = 17.23 \text{ KVAR} ; \text{ similarly } AC = 19.8 \tan(11.48) = 4$$

$$BC = AB - AC \rightarrow BC = 17.23 - 4 = 13.23 \text{ KVAR}$$

$$BC = Q_C ;$$

$$Q_C = 13.23 \text{ KVAR}$$

This is the total KVA required

- The capacity of the capacitor

Since in the capacitive circuit: $I = V/X_C$,

Multiplying both side by V so that

$$Q_C = VI = \frac{V^2}{X_C} \text{ (Volt ampere reactive)}$$

$$\text{Thus } X_C = \frac{V^2}{Q_C} = \frac{220^2}{13230} = 3.66 \Omega$$

$$C = \frac{1}{2\pi f X_C}$$

$$;C = \frac{1}{2\pi \times 60 \times 3.66};$$

$$C = 725 \mu F$$