## COMMON ENRANCE EXAMINATION 1<sup>st</sup> YEAR 1<sup>st</sup> CYLCE (ENSET\_BAMBILI)

Department: Electrical and Power Engineering

**Option: F2 (Electronic) Paper (Major): Electronics**  Session: 2011 Duration: 3hrs Coefficient: 4

Instructions: Choose the good answer, each question carries 1mark.

**EXERCISE 1:** Turn on and Turn off of SCR (silicon controlled rectifier)

 $i_{GT} = 50 mA$ ,  $i_L = 50 mA$ ,  $tgt = 5 \mu s$ ,  $tq = 100 \mu s$ 

When the SCR is on:  $U_{AK} = 1.5V$ ,  $U_{GK} = 1V = RG = 100\Omega$ 

- 1. What is the minimal value of  $E_0$  which can turn on the SCR
- 2.  $E_0$  Equals to 15V. Which has to be the minimal value of  $T_0$  so that SCR starts?
- 3. The impulse of trigger is supposed to be sufficient to turn on the thyristor, the continue voltage U= 120V. Which value must have Rc so that the SCR starts or turn on?
- 4. The SCR (thyristor) to turn it off, a device applies a voltage  $U_{AK} = -V_{EM}$  for a time T. what is the minimal value of T to success the blockage?

EXERCISE 2: Using of Operational Amplifier

rex

- 1) What is the functioning domain of this opamp? Justify your answer.
- 2) Give the definition of offset voltage
- 3) How can we adjust this offset voltage?
- 4) Analyze the diagram and give its function

## Exercise 3: Stabilization zener

The characteristic of the zener diode in reverse polarization (after breakdown) is comparable with a diode passing by the points ( $I_z = 200$ mA,  $U_z = 6.2$ V) and ( $I_z = 100$ mA,  $U_z = 7$ V). It is admitted that the diode functions out of stabilization of tension if  $I_z$  lies between 5mA and 100Am.

- a) Determine the equation of the useful characteristic of the zener diode
- b) In load study( $Rc = 100\Omega$ )

c) Calculate I, J,  $I_z$  and U for e = 18V and  $R = 10 \Omega$  between which limits RC can it vary so that the diode functions in its useful zone (e = 18V and  $R = 100 \Omega$ )?

## Exercise 4: Bipolar Transistor

- 1. Give the equation of attack (input line) and the equation of static load line or continues made of the first stage
- 2. Determine the output quiescent point of the first stage (VBE = 0.7V).
- 3. Deduce the dynamic line load of the second stage
- 4. Give the equivalent diagram of the amplifier in small signals or dynamics (Bypass emitter)
- 5. Calculate the voltage amplification  $A_{v1}$ ,  $A_{v2}$  respectively of the first and second stage
- 6. Deduce the total amplification  $A_v$

## COMMON ENRANCE EXAMINATION 1<sup>st</sup> YEAR 1<sup>st</sup> CYLCE (ENSET\_BAMBILI)