

COMMON ENTRANCE EXAMINATION 1st YEAR 1st CYLCE (ENSET_BAMBILI)

Department: Electrical and Power Engineering

Session: 2013

Option: F2 (Electronic)

Duration: 3hrs

Paper (Major): Electronics

Coefficient: 4

Instructions: Choose the good answer, each question carries 1mark.

1. Which is the most widely used semiconductor?
 - a) Copper
 - b) Germanium
 - c) Silicon
 - d) None of the above
2. How many protons does the nucleus of a silicon atom contain
 - a) 4
 - b) 14
 - c) 29
 - d) 32
3. How many valence electrons does a Germanium atom have?
 - a) 0
 - b) 1
 - c) 2
 - d) 4
4. In an pnp transistor, the majority carriers in the base are
 - a) Free electrons
 - b) Holes
 - c) Neither
 - d) Both
5. The nucleus of a copper atom contains how many protons?
 - a) 1
 - b) 4
 - c) 18
 - d) 29
6. Holes are the majority carriers in which type of semiconductors?
 - a) Extrinsic
 - b) Intrinsic
 - c) N – type
 - d) P – type
7. What is the barrier potential of a silicon diode at room temperature?
 - a) 0.3
 - b) 0.7
 - c) 1V
 - d) $2mV/C^0$
8. A reverse voltage of 20V is across a diode. What is the voltage across the depletion layer?
 - a) 0V
 - b) 0.7V
 - c) 20V
 - d) None of the above
9. The knee voltage of a diode is approximately equal to the:
 - a) Applied voltage
 - b) Barrier potential

- c) Breakdown voltage
 - d) Forward voltage
10. If $N_1/N_2 = 2$, and the primary voltage is 120V, what is the secondary voltage?
- a) 0V
 - b) 36V
 - c) 40V
 - d) 60V
11. In a step down transformer, which is larger?
- a) Primary voltage
 - b) Secondary voltage
 - c) Neither
 - d) No answer possible
12. We want a peak load voltage of 40V out of bridge rectifier. What is the approximate rms value of secondary?
- a) 28.28V
 - b) 14.4V
 - c) 28.3V
 - d) 56.6V
13. If line frequency is 50Hz, the output frequency of a half wave rectifier is:
- a) 1f
 - b) 50Hz
 - c) 100hz
 - d) 50Hz
14. If the filtered load current is 10mA, which of the following has a diode current of 10mA?
- a) Half wave rectifier
 - b) Full wave rectifier
 - c) Bridge rectifier
 - d) Impossible to say
15. If the filter capacitance is increased, the ripple will:
- a) Decrease
 - b) Stay the same
 - c) Increase
 - d) None of these
16. What is true about the breakdown voltage in a zener diode?
- a) It decrease when current increases
 - b) It destroys the diode
 - c) It equal the current times the resistance
 - d) It is approximately constant
17. Which of these is the best description of a zener diode?
- a) It is a diode
 - b) It is a constant current device
 - c) It is constant voltage device
 - d) It works in the forward region
18. A zener diode
- a) Is a battery
 - b) Acts like a battery in the breakdown region
 - c) Has a barrier potential of 1V
 - d) Is forward biased
19. If the load resistance decreases in a zener regulator, the current:
- a) Decreases

- b) Stays the same
- c) Increased
- d) Equals the source voltage divided by the series resistance

20. The voltage across the zener resistance is usually:

- a) Small
- b) Large
- c) Measured in volts
- d) Subtracted from the breakdown voltage

brainprepa